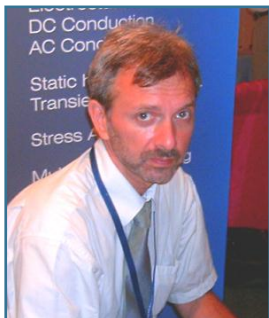




Simulation of power transmission lines in QuickField



Vladimir Podnos
Director of Marketing and Support
Overview of QuickField capabilities



Alexander Liubimtsev
Support engineer
QuickField live presentation:
power transmission line simulations



QuickField Analysis Options

Magnetic Suite

AC Magnetics

Transient + DC Magnetics

DC Magnetics

Electric Suite

AC conduction + Electrostatics & DC conduction

Transient Electric + Electrostatics & DC conduction


Electrostatics & DC conduction

Thermostructural

Stress Analysis

Transient Heat transfer

Steady State Heat transfer


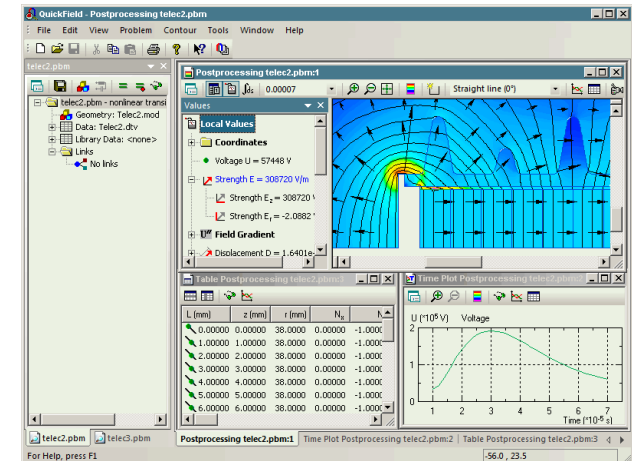




MultiPhysics


Temperature
Field

Electromagnetic
fields

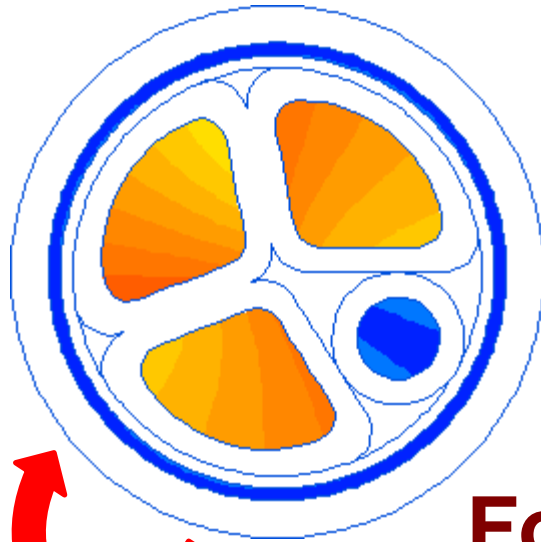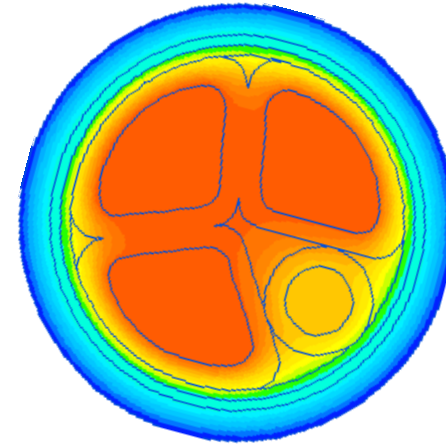

Thermal
Stresses

Forces

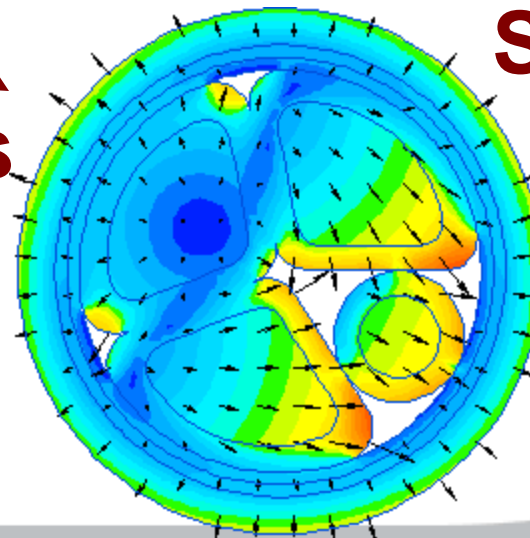


Magnetic state
import

Stresses &
Deformations




QuickField solvers

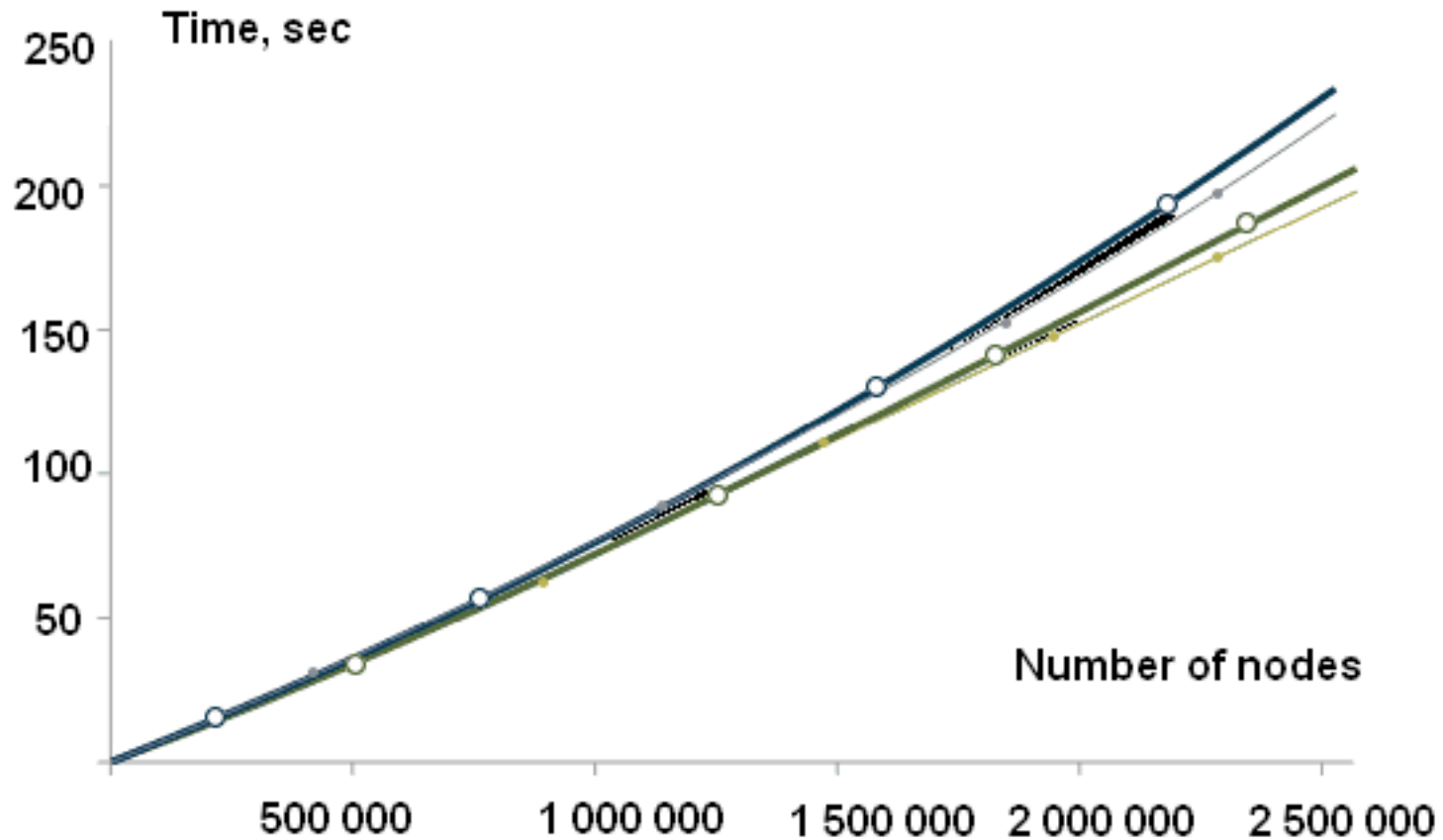Solution time for various sizes of finite element mesh





Open object interface

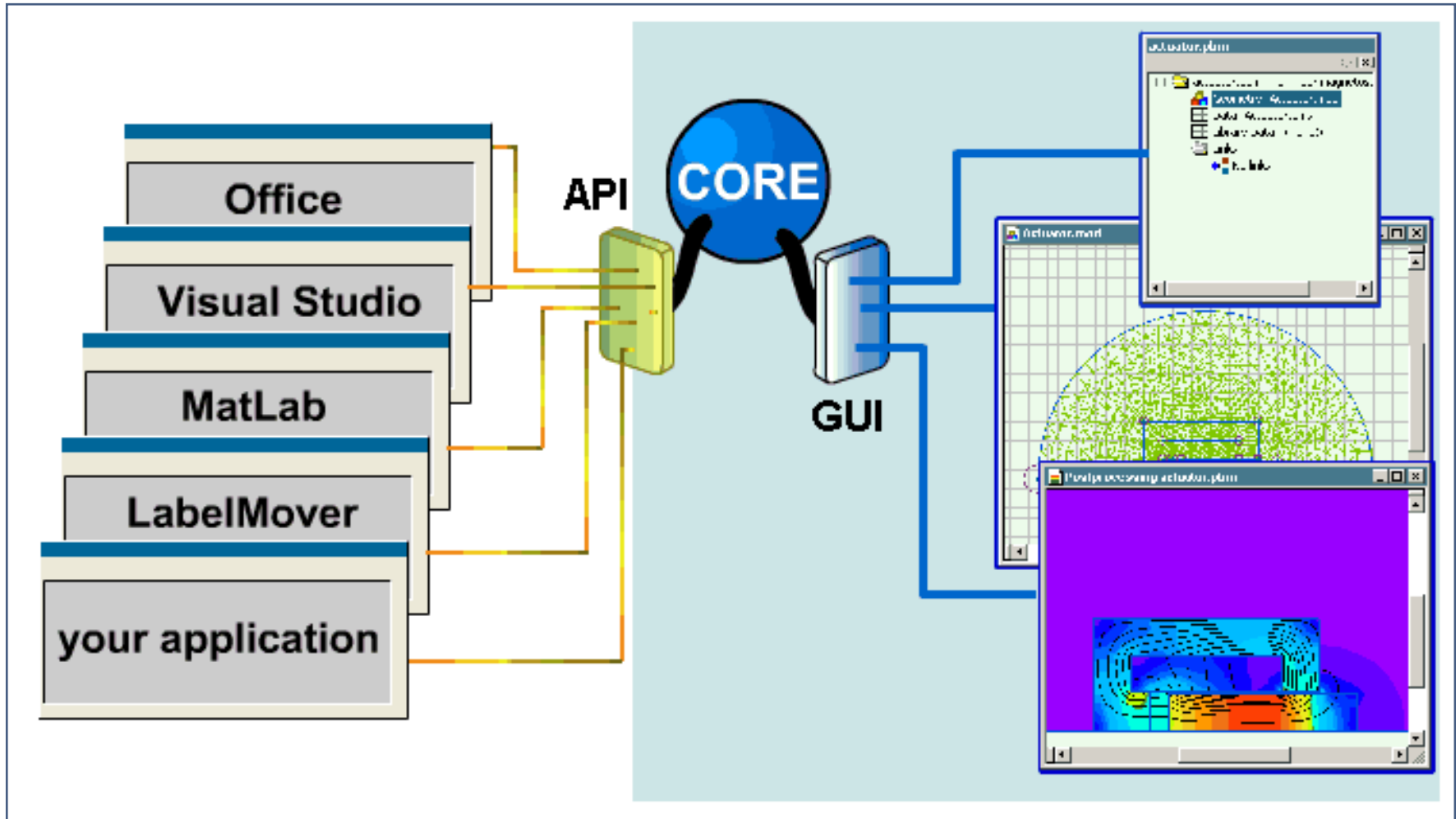



ActiveField API object model

ActiveField™ help

[Main QuickField Site](#)

[Free Downloads](#)

[Contacts](#)


- [ActiveField Technology](#)
- [Objects Overview](#)
- [Hierarchy Chart](#)
- [How to Start: Application Object](#)
- [How to work with Problems](#)
- [How to work with Model](#)
- [How to work with Data](#)
- [How to Analyze Results](#)

Objects

Properties

Methods

QuickField Object Model

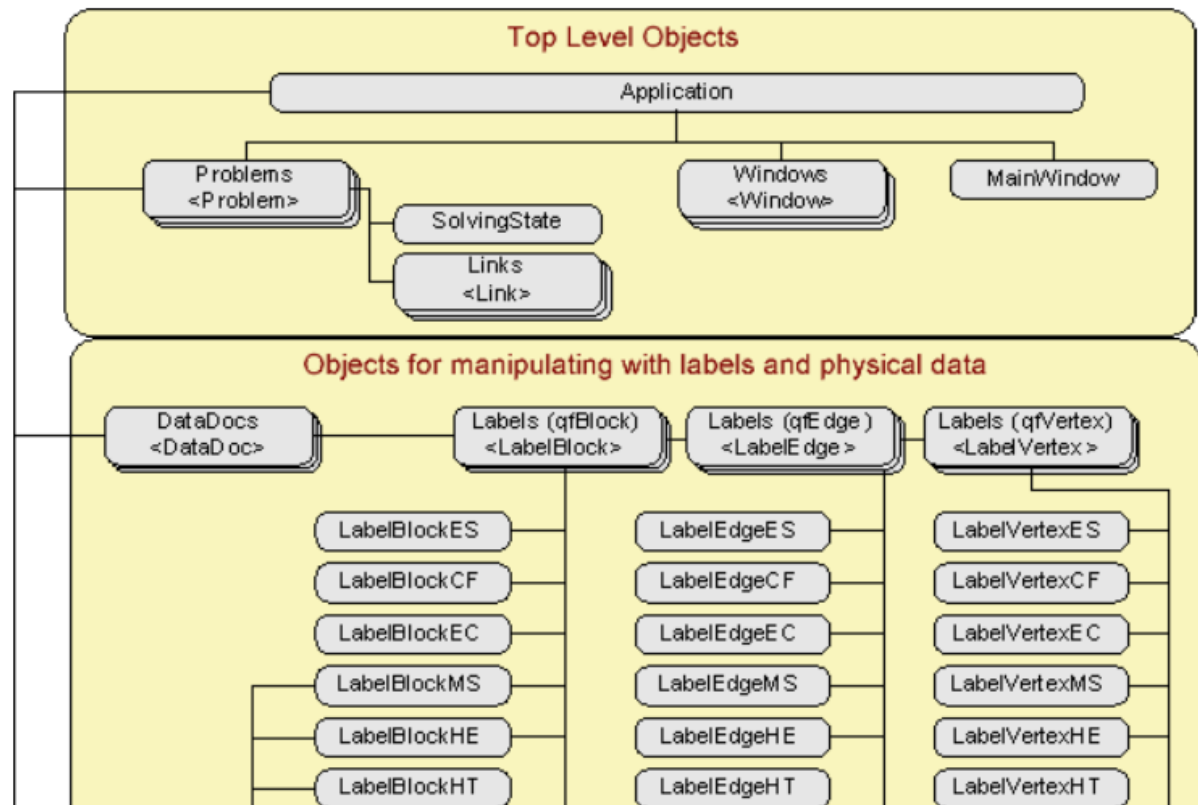




QuickField Difference





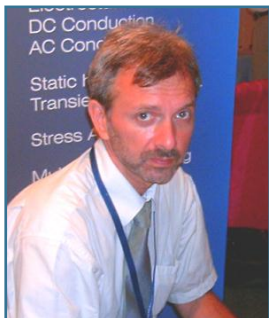Simulation of power transmission lines in QuickField



Vladimir Podnos
Director of Marketing and Support
Overview of QuickField capabilities



Alexander Liubimtsev
Support engineer
QuickField live presentation:
power transmission line simulations




Simulation of power transmission lines in QuickField

1. Parallel wires capacitance.
2. Transmission line capacitance.
3. Fiber-optic cable and electric transmission line.
4. Parallel wires inductance.
5. Transmission line transposition.
6. Phase-to-phase fault.
7. Disc insulator. Heating.
8. Disc insulator. Mechanical stress.



Parallel wires capacitance

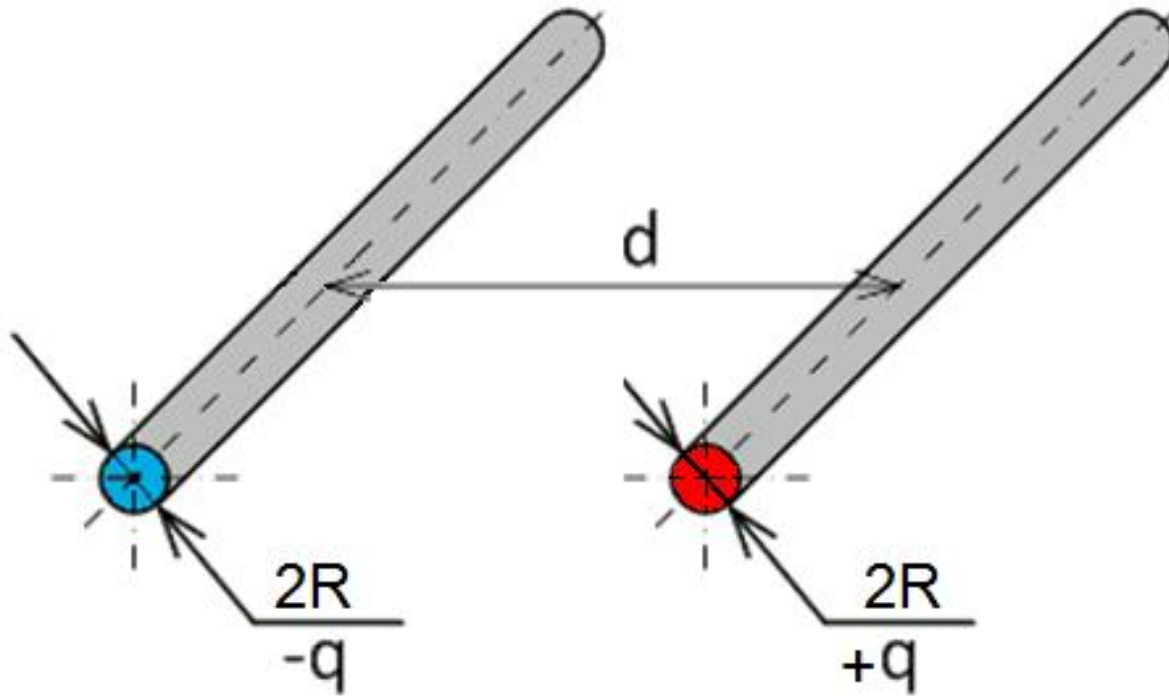

Given:

$$D = 0.5 \text{ m}$$

$$R = 0.005 \text{ m.}$$

Calculate:


Capacitance
between two wires

$$C = q / (U_2 - U_1)$$

$$C = \frac{\pi \epsilon}{\ln \left(\frac{D}{2 \cdot R} + \sqrt{\frac{D^2}{4 \cdot R^2} - 1} \right)} = 6,0375 \text{ [uF/km]}$$



Transmission line capacitance

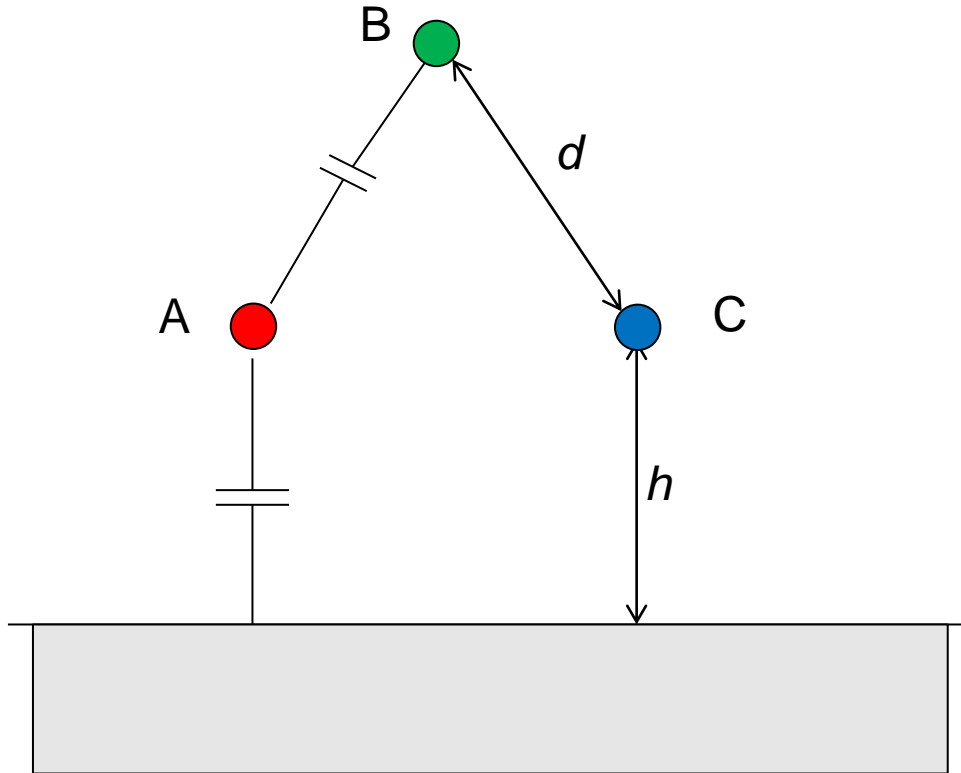

Given:

Line voltage (RMS) $U = 10 \text{ kV}$

$d = 1 \text{ m}$

$h = 6 \text{ m}$

Calculate:


Self and mutual capacitances.

$$U_a = C_{aa}^* q_a + C_{ab}^* q_b + C_{ac}^* q_c$$

C^* - potential coefficient [1/F]



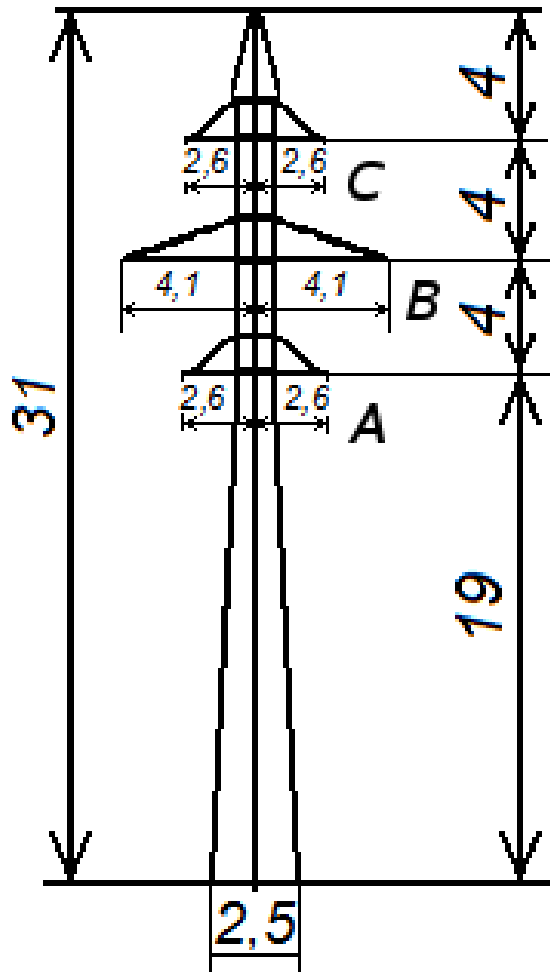Fiber-optic cable and electric transmission line



Given:


Line voltage (RMS) $U = 110$ kV

Calculate :

Electric field strength



Parallel wires inductance

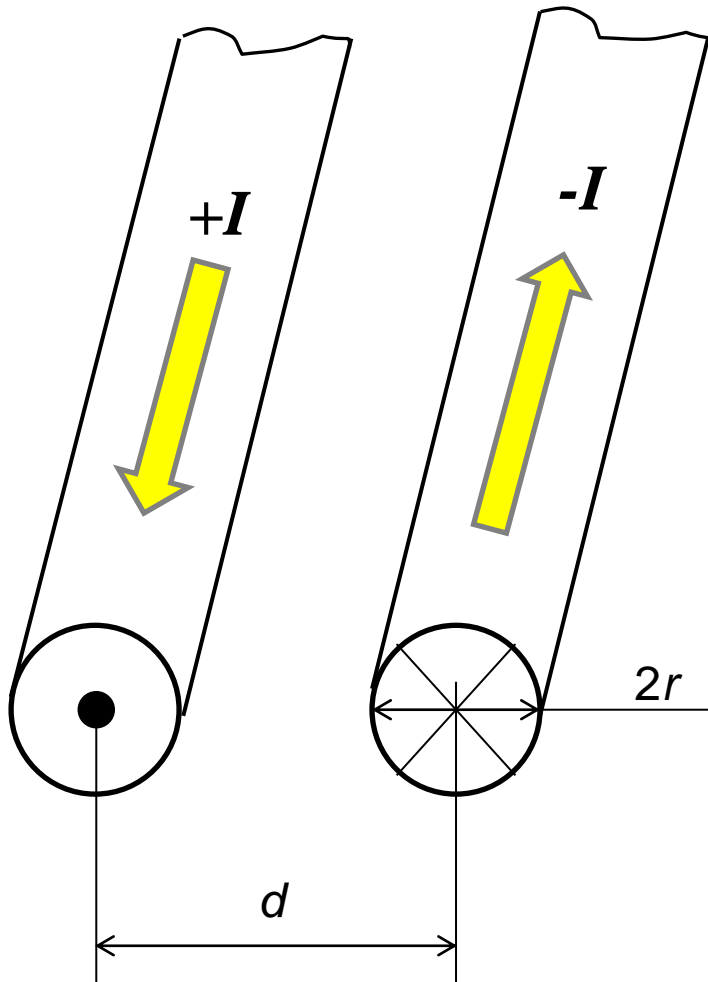

Given :

$$d = 0.5 \text{ m}$$

$$r = 0.005 \text{ m}$$


Calculate :

Inductance between the wires $L = \Phi / I$ [H/m]

$$L = \mu_0 / \pi [\ln(d/r) + 0.25] = 1.94 \text{ mH/km}$$



Transmission line transposition

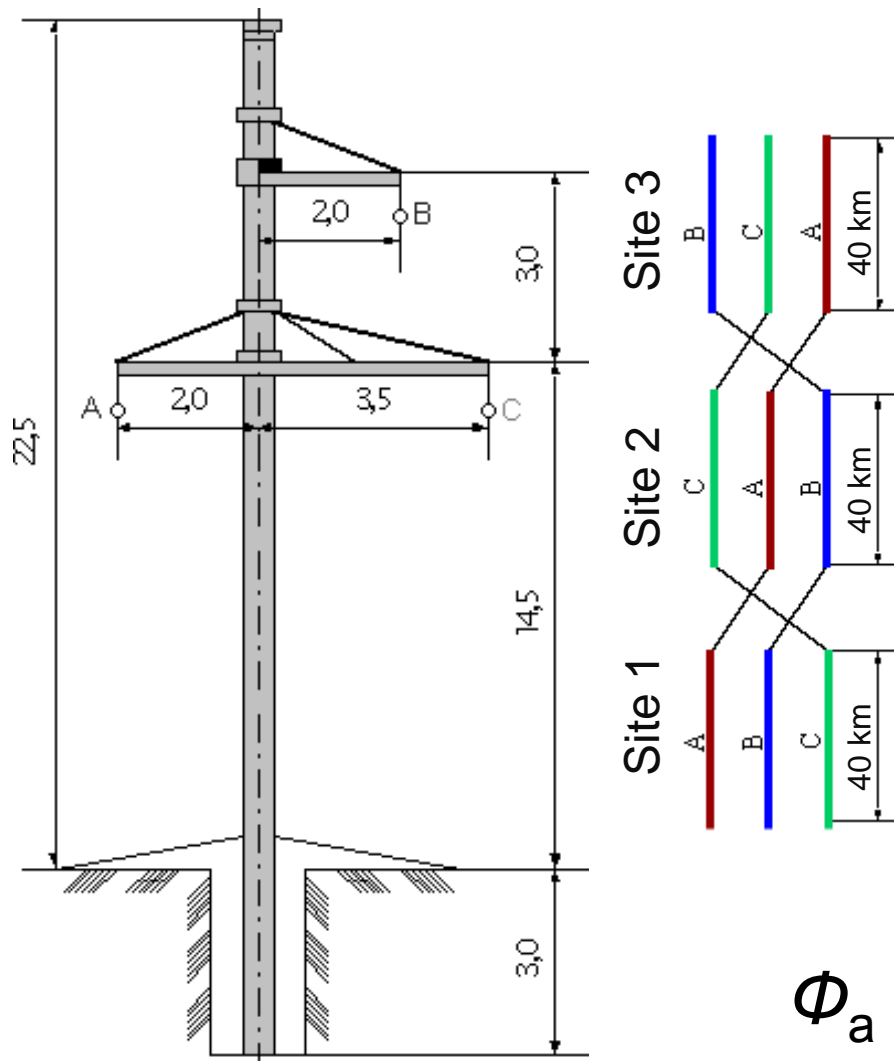

Given :

Line voltage (RMS) $U = 110$ kV

Length of the line = 120 km

Load:

$R_l = 100 \Omega$,

$L_l = 72.3 \Omega$ (0.23 H).


Calculate :

Inductances.

$$\Phi_a = L_{aa} * I_a + M_{ab} * I_b + M_{ac} * I_c$$



Phase-to-phase fault

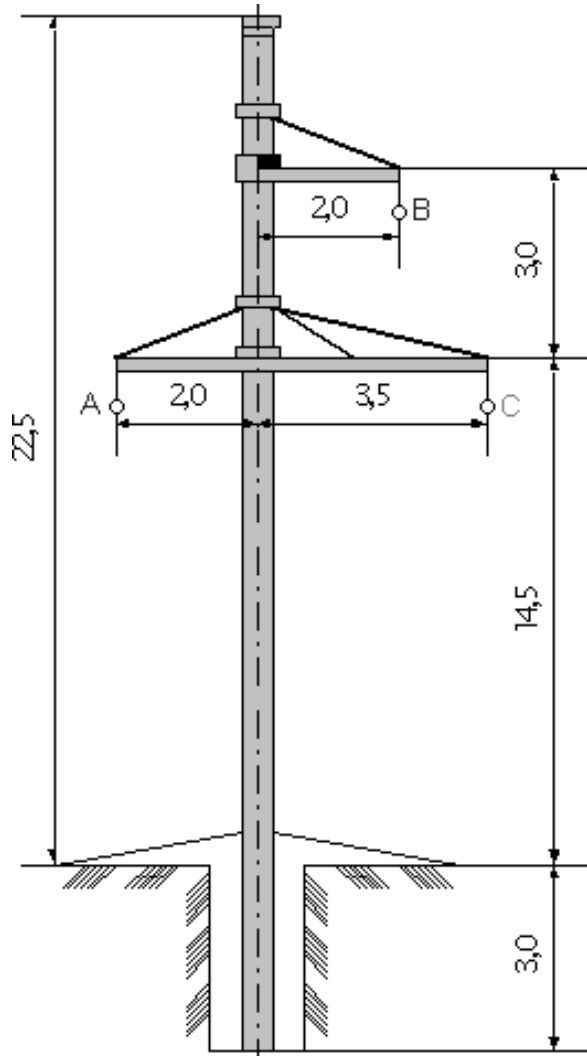


Given :

Line voltage (RMS) $U_{pp} = 110$ kV

Length of the line = 20 km

Internal impedance of the source:

$R = 1 \Omega$, $L = 0.02$ H.

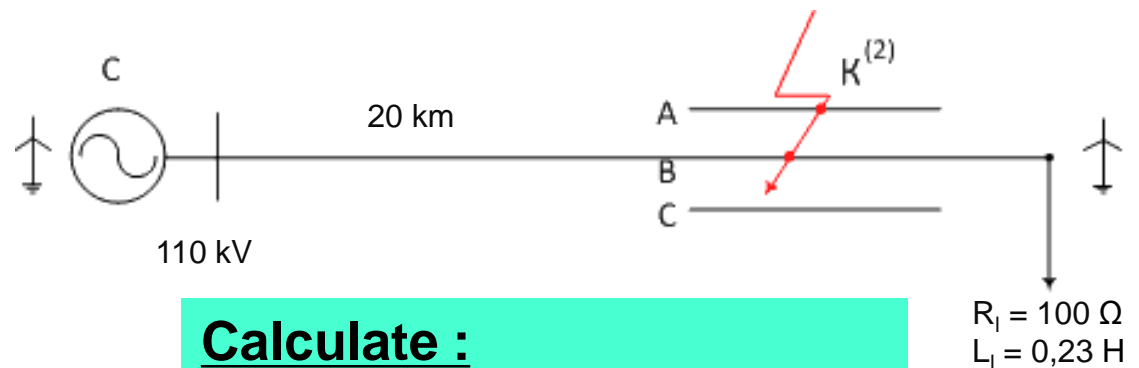


Calculate :

Short circuit currents.

Ampere forces.



Disc insulator. Heating

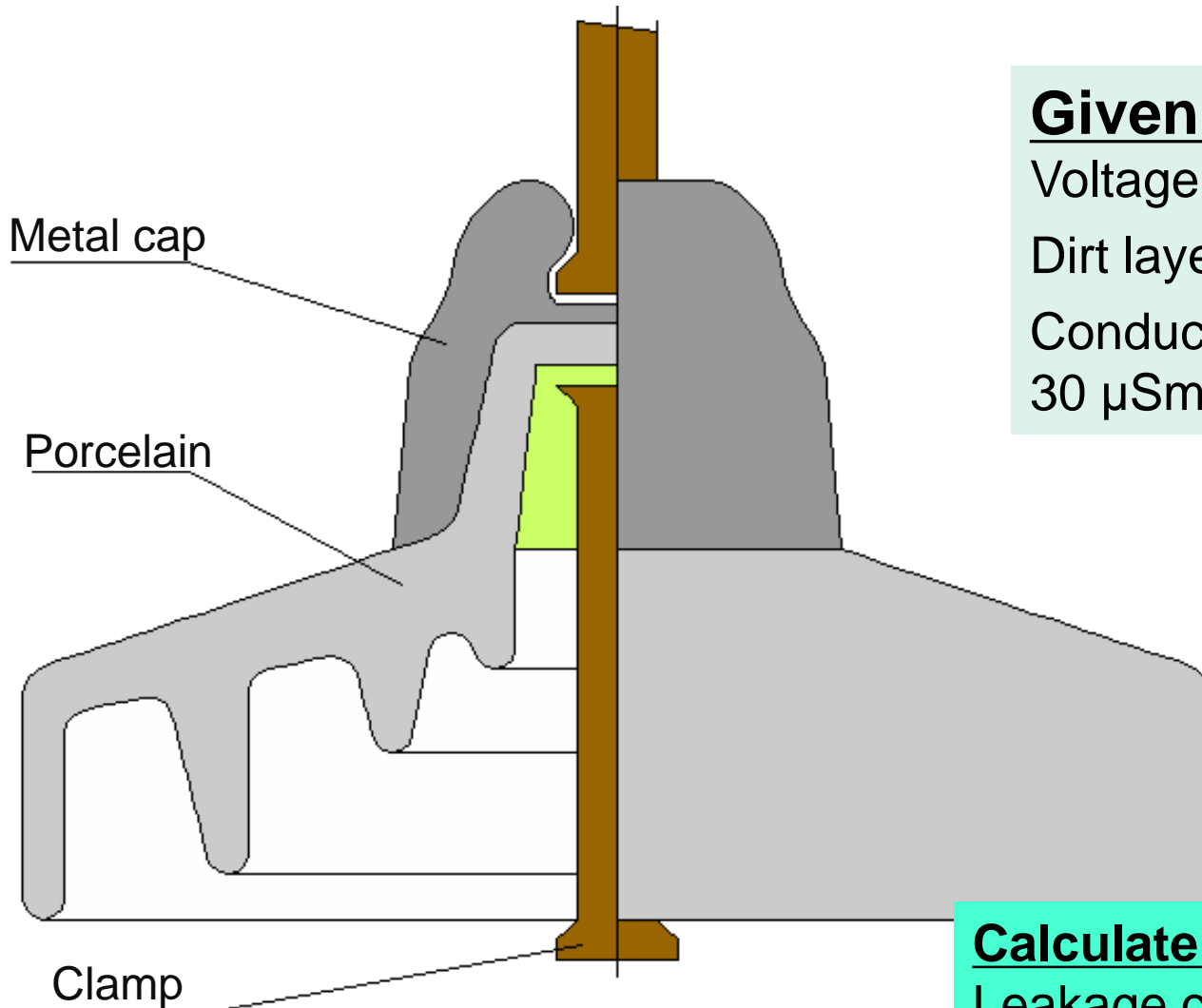

Given :

Voltage = 10 kV

Dirt layer thickness = 1 mm.


Conductivity of the layer
 $30 \mu\text{Sm/cm}$.

Calculate :

Leakage currents, Power of losses, insulator temperature



Disc insulator. Stress

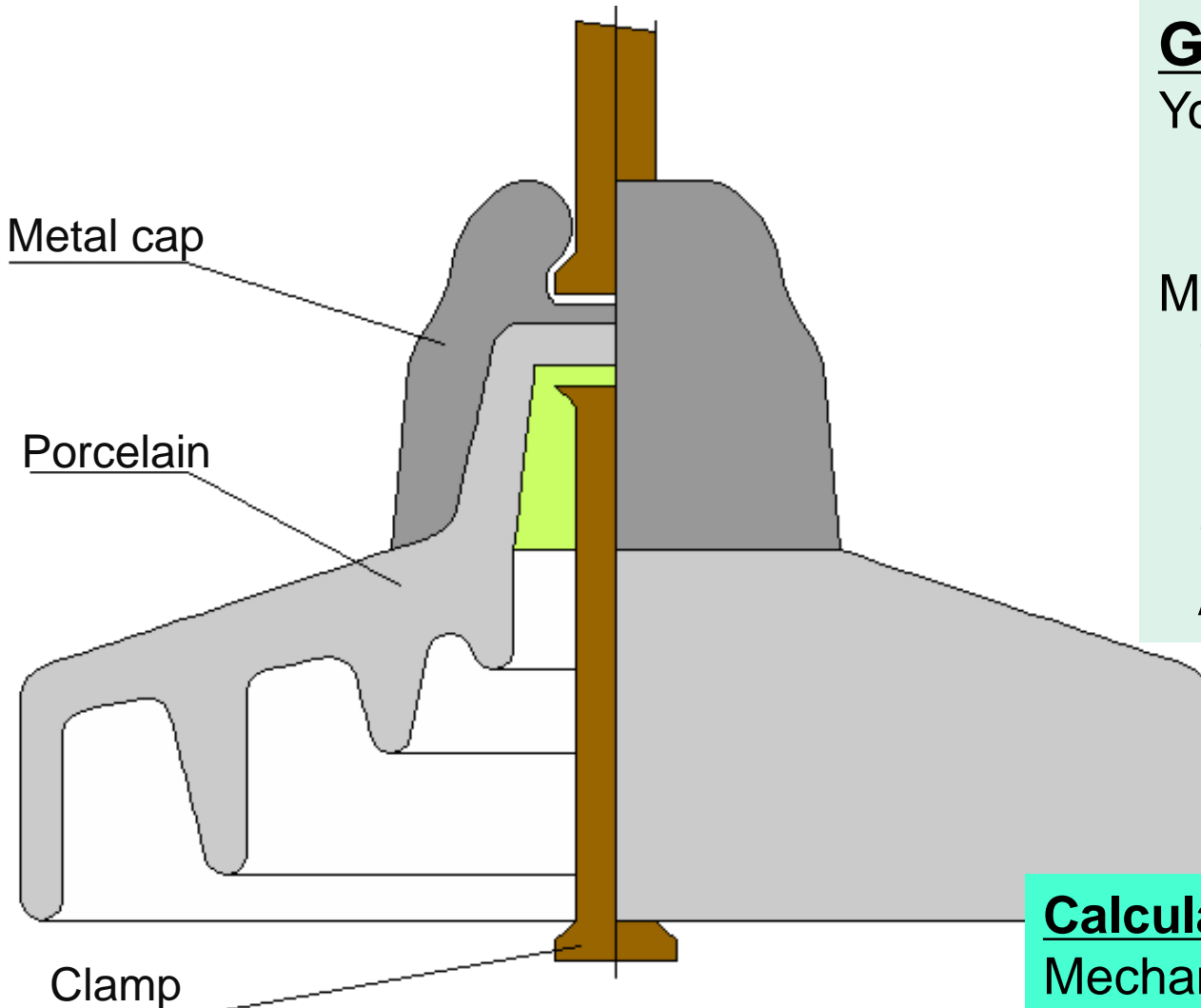

Given:

Young modulus:
steel 210 GPa,
porcelain 59 GPa.

Mechanical load:

wire weight	900 N
ice weight	600 N
insulators	300 N
wind force	800 N
Ampere force	200 N

Calculate :

Mechanical stresses in insulator